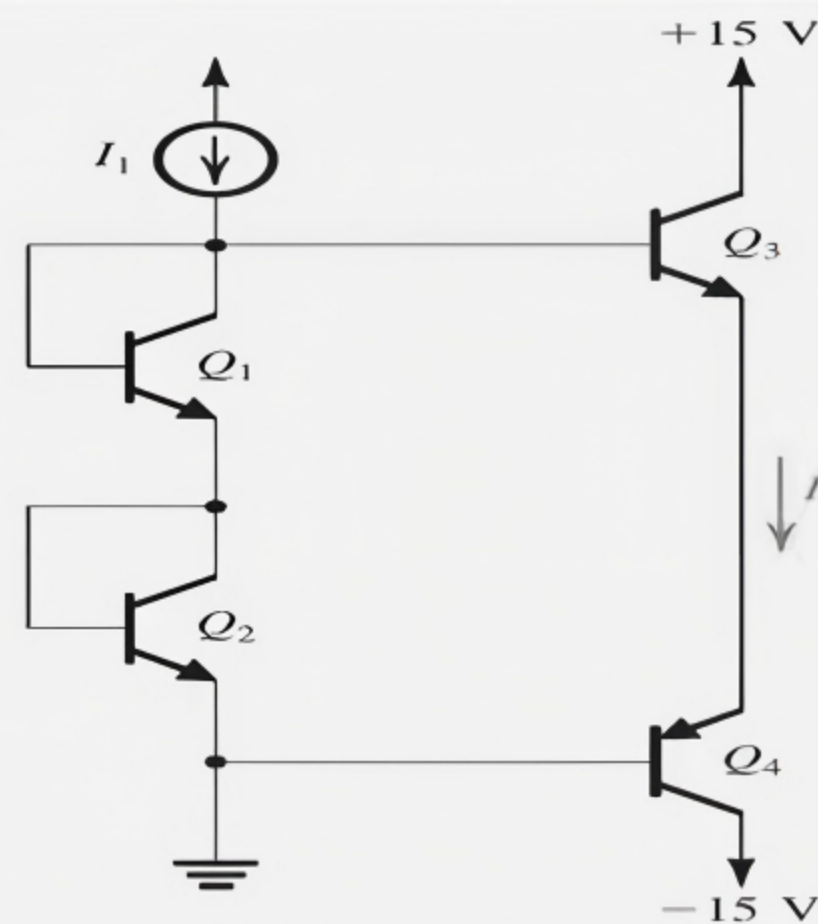




<think>

<location>[{"name": "Ω4", "box": [247, 213, 295, 256], "type": "nprn"}]</location>

<trace>[{"id": "wire_1", "start": {"name": "Ω4", "coord": [248, 234]}, "key_points": [[92, 155], [63, 77], [62, 155], [92, 191], [123, 154]], "end": [{"name": "Q2", "coord": [91, 187]}, {"name": "Q1", "coord": [91, 139]}, {"name": "Q3", "coord": [248, 88]}]}, {"id": "wire_2", "start": {"name": "Ω4", "coord": [294, 234]}, "key_points": [[306, 234]], "end": []}, {"id": "wire_3", "start": {"name": "Ω4", "coord": [280, 255]}, "key_points": [], "end": [{"name": "-15V port", "coord": [280, 270]}]}]</trace>

By organizing the end points, I know Ω4 connects to -15V port, Q1, Q2, Q3. Based on the identified connections, the valid options are A, C, D

</think>

<answer>A, C, D</answer>



Question: Identify all devices connected to Ω4. Select all that apply.

A. Q3 B. I1 C. Q2 D. Q1